

c) There are now ‘more places’ to put the charge. If C is already charged up, and we add $2C$ in parallel, we have just added another path for current to take, so current will now start to flow through the battery again to create a charge distance on the new capacitor, which increases the total amount of charge you can store for a given potential difference!

d) Imagine that the top plate of the C capacitor is positive. The middle arrangement of the bottom plate of the C capacitor, the top plate of the $2C$ capacitor, and the connecting wire is initially neutral, and *isolated*, so the net charge will always be zero. The positive charges on the top plate of C and the negative charges on the bottom plate of $2C$ ‘push’ and ‘pull’ electrons from the bottom plate of the middle segment to the top plate of the middle segment, leaving the net charge zero and creating a charge separation - up to the point that there will be a net charge $-Q$ on the top plate (i.e. the bottom plate of the C capacitor) and a net charge $+Q$ on the bottom plate (i.e. the top plate of the $2C$ capacitor). The charges on C and $2C$ are therefore equal in size.

e) $V_{\text{left}} = V = 12\text{V}$ $V_{\text{right}} = V = 12\text{V} = V_{\text{left}}$
 $Q_{\text{left}} = CV = 2.4 \times 10^{-5} \text{ coul}$ $Q_{\text{right}} = 2CV = 4.8 \times 10^{-5} \text{ coul}$

f) $Q_{\text{top}} = 2/3 CV = 1.6 \times 10^{-5} \text{ coul}$ $Q_{\text{bottom}} = 2/3 CV = 1.6 \times 10^{-5} \text{ coul}$
 $V_{\text{top}} = Q_{\text{top}} / C = 8 \text{ V}$ $V_{\text{bottom}} = Q_{\text{bottom}} / 2C = 4 \text{ V}$
 Note that the total voltage drop across both capacitors, $V_{\text{top}} + V_{\text{bottom}}$, is the same as the voltage across the battery, $V = 12\text{V}$. This is one of Kirchhoff's Rules.

4. a) The two 2 Farad capacitors (which we will label C_{top} and C_{bottom}) can be considered as in series with each other. If we treat the two rightmost capacitors (the ones in series) as one equivalent capacitor, then that equivalent capacitor can be considered to be in parallel with the 4 Farad capacitor (which we will label C_{left}).

b) $V_{\text{batt}} = V_{\text{left}} > V_{\text{top}} = V_{\text{bottom}} = V_{\text{batt}} / 2$

c) $Q_{\text{left}} = 1.5 \text{ coul}$ $V_{\text{left}} = Q_{\text{left}} / C_{\text{left}} = 0.375 \text{ V}$
 $Q_{\text{top}} = V_{\text{top}} C_{\text{top}} = 0.375 \text{ coul}$ $V_{\text{top}} = V_{\text{left}} / 2 = 0.1875 \text{ V}$
 $Q_{\text{bottom}} = Q_{\text{top}} = 0.375 \text{ coul}$ $V_{\text{bottom}} = V_{\text{top}} = 0.1875 \text{ V}$
 Note that we used $V_{\text{left}} = V_{\text{top}} + V_{\text{bottom}}$, and then used the symmetry of the top and bottom capacitors to say that $V_{\text{top}} = V_{\text{bottom}}$ and thus that $V_{\text{top}} = V_{\text{left}} / 2$.

d) $V_{\text{batt}} = V_{\text{left}} = V_{\text{top}} + V_{\text{bottom}} = 0.375\text{V}$

e) (i) $U = U_{\text{left}} + U_{\text{top}} + U_{\text{bottom}} = 0.281 \text{ J} + 0.035 \text{ J} + 0.035 \text{ J} = 0.351 \text{ J}$

(ii) $C_{\text{equiv}} = C_{\text{left}} + \left(\frac{1}{C_{\text{top}}} + \frac{1}{C_{\text{bottom}}} \right)^{-1} = 4 \text{ Farad} + 1 \text{ Farad} = 5 \text{ Farad}$
 $U = C_{\text{equiv}} V_{\text{batt}}^2 / 2 = 0.351 \text{ J}$